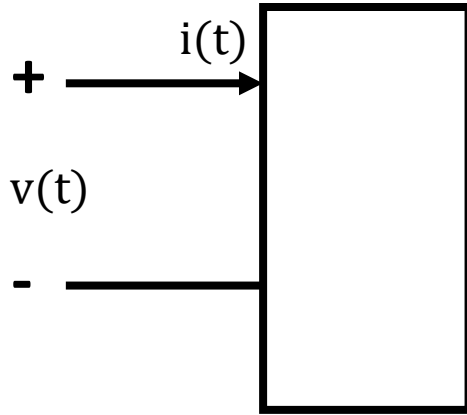


Power sources and elements

Charge, Current, Voltage, Power

q $\frac{dq}{dt}$ $v(t)$ $p(t)$







Power absorbed

$P(t) = V(t)I(t) > 0$ if either $V(t), I(t) > 0$ or $V(t), I(t) < 0$

Independent Sources





Voltage

Current

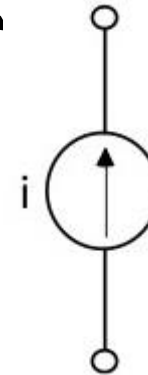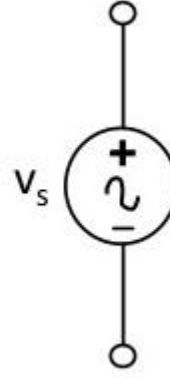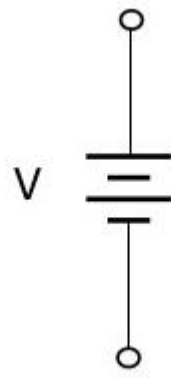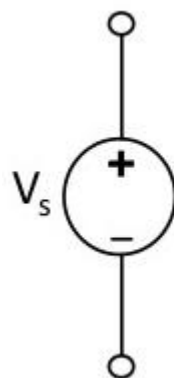

Power sources and elements

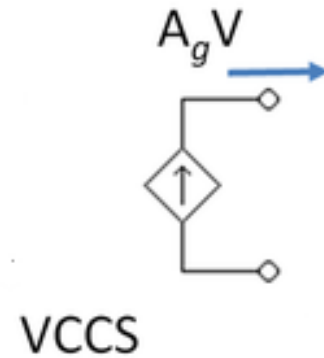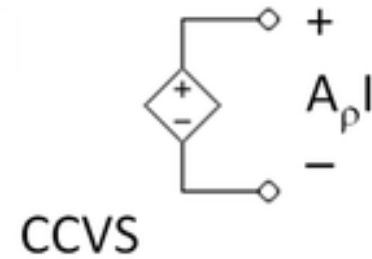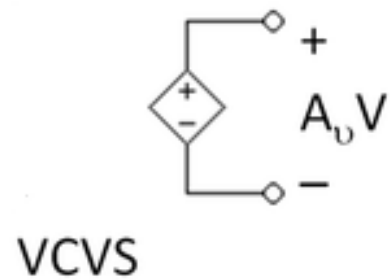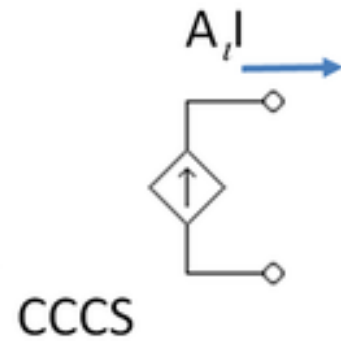
Dependent Sources:
current / voltage controlled current / voltage sources



Kirchhoff's Laws

Kirchhoff's current law (KCL)

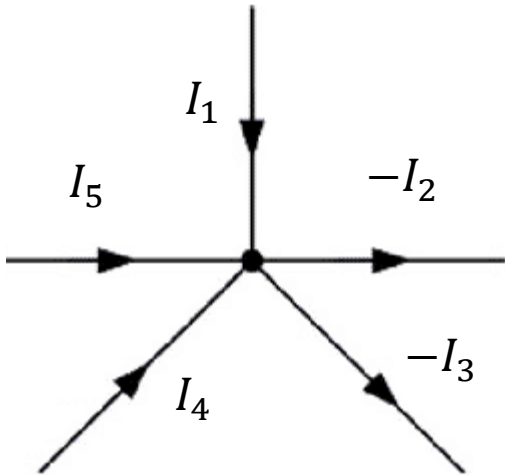- A consequence of *charge* conservation
- Node: a point where two or more elements meet




$$\sum_{j=1}^n I_j = 0$$

(KCL)

Kirchhoff's voltage law (KVL)

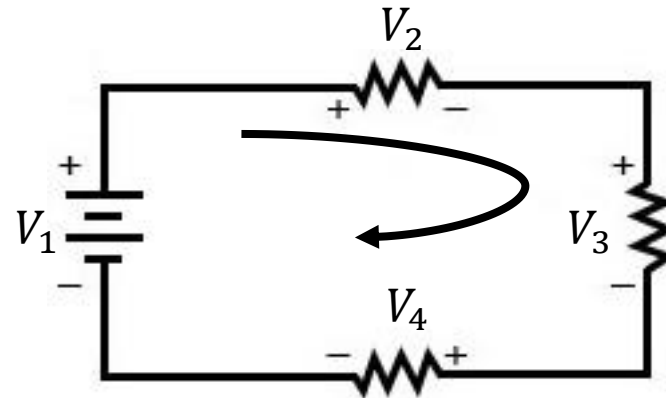
- A consequence of *energy* conservation
- Loop: a closed path starting from a particular node and ending there *without* revisiting that particular node



$$\sum_{i=2}^m V_i = V_1$$

(KVL)

Resistors in series and in parallel

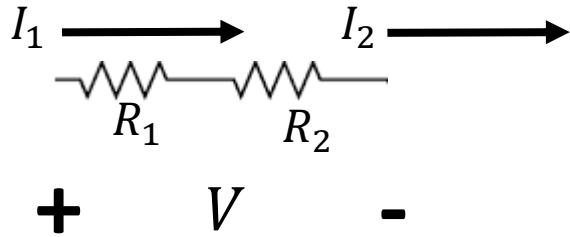


$I_1 = I_2 = I$ (suppose) by KCL

$$V = I_1 R_1 + I_2 R_2 = I(R_1 + R_2)$$

$$\frac{V}{I} = R_1 + R_2$$

The equivalent resistance for n resistors by induction will be given by

$$R_{eq} = \sum_{i=1}^n R_i$$

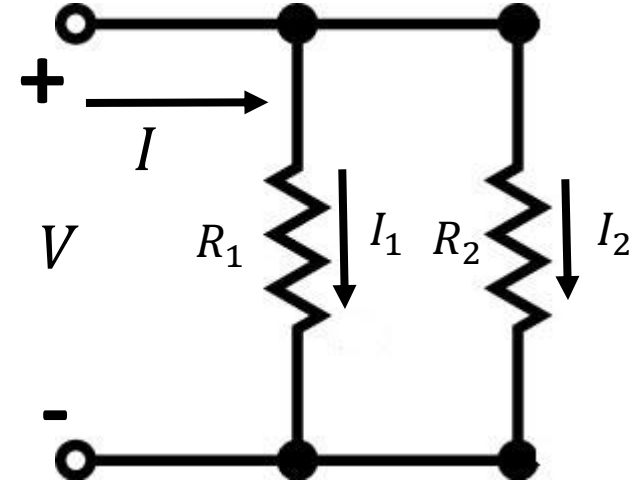

$$V = I_1 R_1 = I_2 R_2$$

$$I_1 + I_2 = I$$

$$V \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = I$$


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

For n resistors,


$$R_{eq} = \left(\sum_{i=1}^n R_i^{-1} \right)^{-1}$$

A similar approach can be followed for finding equivalent Inductance in series and parallel

Capacitors in series and in parallel

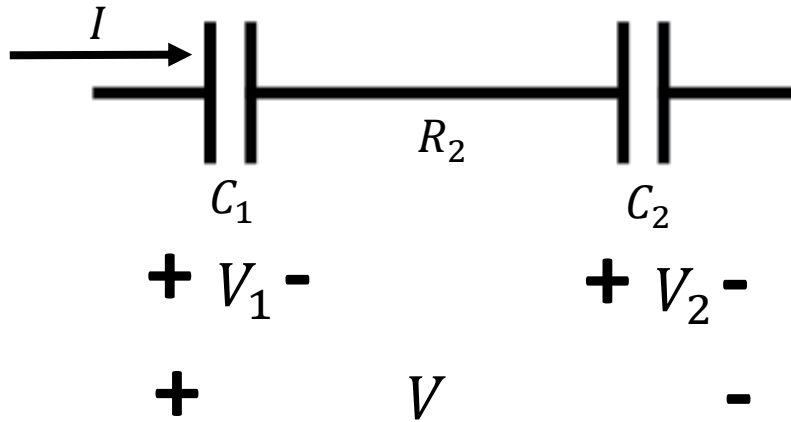

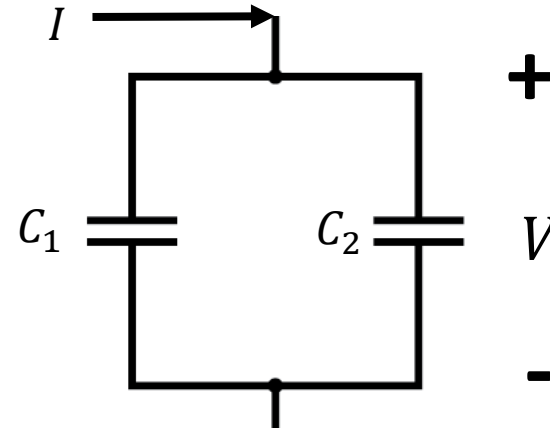
$$\begin{aligned}
 I &= C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt} \quad (\text{KCL}) \\
 I \left(\frac{1}{C_1} + \frac{1}{C_2} \right) &= \frac{d(V_1 + V_2)}{dt} = \frac{dV}{dt} \\
 I &= \frac{C_1 C_2}{C_1 + C_2} \frac{dV}{dt} \\
 C_{eq} &= \frac{C_1 C_2}{C_1 + C_2}
 \end{aligned}$$




$$\begin{aligned}
 I &= I_1 + I_2 = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_2}{dt} \\
 I &= (C_1 + C_2) \frac{dV}{dt} \\
 C_{eq} &= C_1 + C_2
 \end{aligned}$$

Voltage and Current division

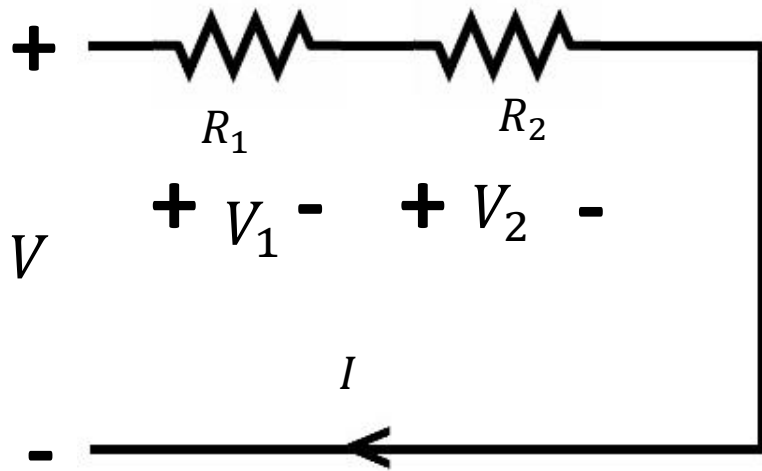

Voltage Division
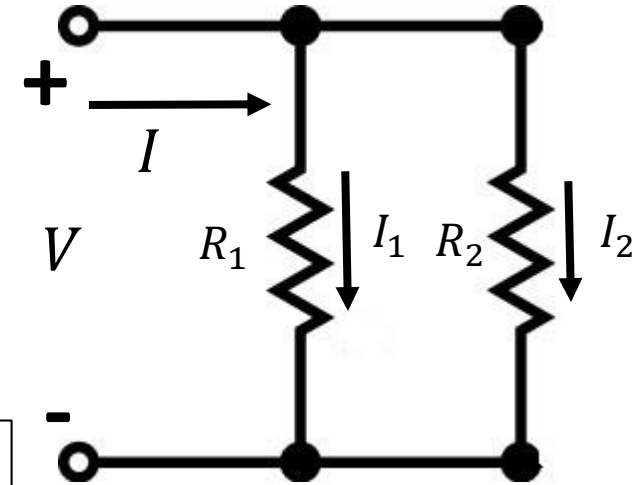
$$I = \frac{V}{R_1 + R_2}$$
$$V_1 = IR_1 = \frac{R_1}{R_1 + R_2} V$$
$$V_2 = IR_2 = \frac{R_2}{R_1 + R_2} V$$



Current Division

$$V = I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}$$

$$I = V \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$V = I(R_1 || R_2)$$

$$I_1 = \frac{I(R_1 || R_2)}{R_1} = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{I(R_1 || R_2)}{R_2} = I \frac{R_1}{R_1 + R_2}$$

Node and Mesh analysis


Node Analysis

- Applicable to all networks
- Choose the node with maximum number of branches as a reference node or the ground node as reference node.
- If there are N nodes, then we use one as ground and for remaining ones provide voltage as $V_1, V_2, V_3, \dots V_{N-1}$.
- We get $N - 1$ equations using KCL
- Presence of a voltage source may force us to merge two nodes into a super node to apply KCL .

Mesh Analysis

- Applicable only to planar networks
- If current source exists then super mesh may be used so that KVL can be applied successfully or define an unknown voltage across the current sources.
- The number of equations formed are equal to number of all the closed loops present in the circuit

Node Analysis Example

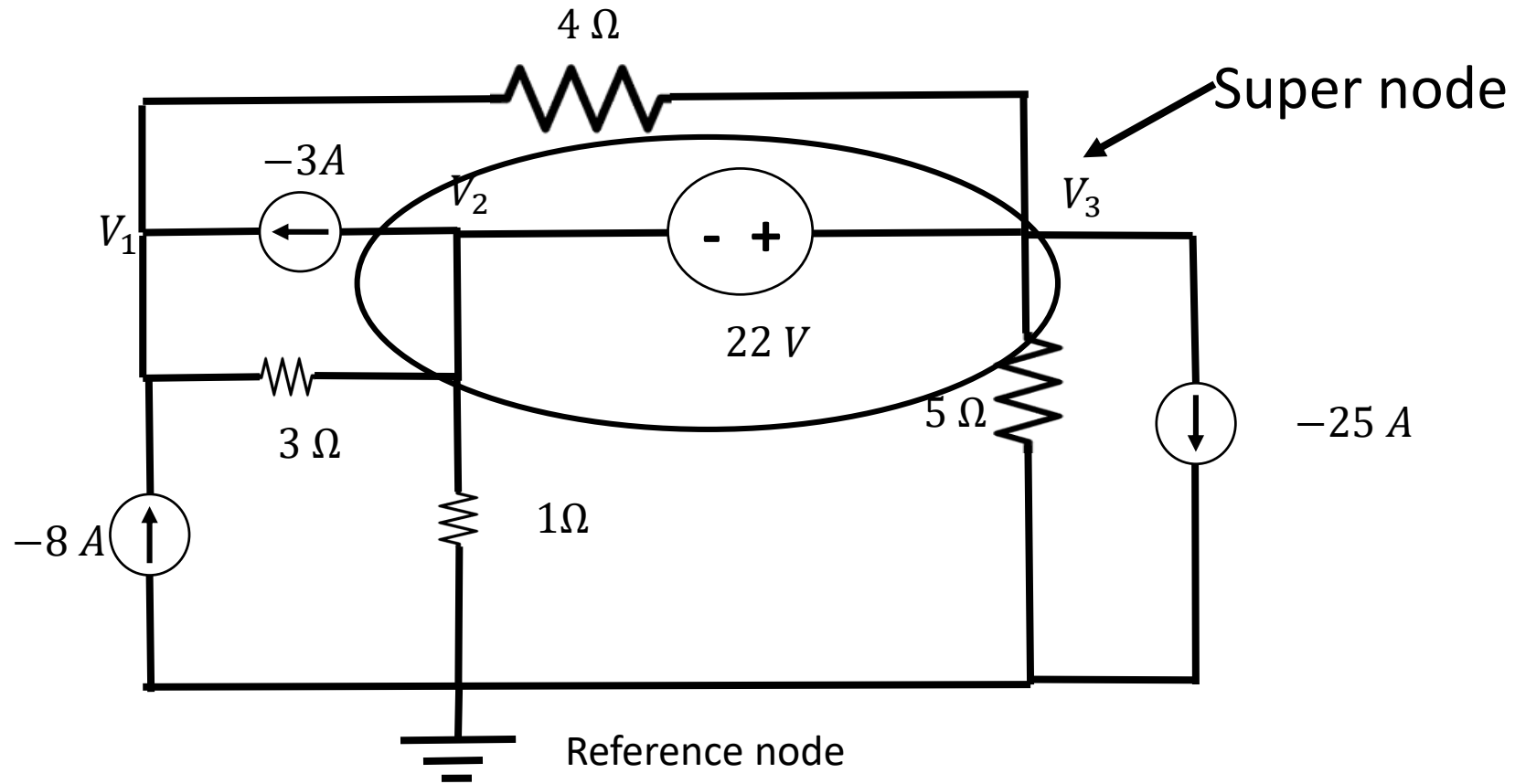

Node Analysis Example

$$\text{KCL at node 1: } -8 - 3 + \frac{V_2 - V_1}{3} + \frac{V_3 - V_1}{4} = 0 \quad (1)$$

KCL at 'super node' (currents entering add up to zero)

$$3 + \frac{V_1 - V_2}{3} - \frac{V_2}{1} - \frac{V_3}{5} + 25 + \frac{V_1 - V_3}{4} = 0 \quad (2)$$

$$V_2 - V_3 = -22 \quad (3)$$

Now we have three equations.

If 22 V source is replaced by a resistor R then no need of super node and

(2) \rightarrow (2') and (3) \rightarrow (3')

$$3 + \frac{V_1 - V_2}{3} - \frac{V_2}{1} + \frac{V_3 - V_2}{R} = 0 \quad (2')$$

$$\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{R} - \frac{V_3}{5} + 25 = 0 \quad (3')$$

Node Analysis Example

If we do not want to define a super node in case 1, then we can define current I from node 2 to node 3, then we will have

$$3 + \frac{V_1 - V_2}{3} - \frac{V_2}{1} - I = 0 \quad \textbf{(Node 2)}$$

$$I + \frac{V_1 - V_3}{4} - \frac{V_3}{5} + 25 = 0 \quad \textbf{(Node 3)}$$


$$\text{And } V_2 - V_3 = 22$$

Now we have 4 variables V_1, V_2, V_3 & I with 4 equations. So there is a trade off. Supernode leads to less number of equations. Similar situation arises for a need of super mesh if \exists a current source.

Add Node 2 and Node 3 equations

$$3 + \frac{V_1 - V_2}{3} + -\frac{V_1 - V_3}{4} - \frac{V_2}{1} - \frac{V_3}{5} + 25 = 0 \quad \textbf{(same as (2))}$$

Supermesh Analysis Example

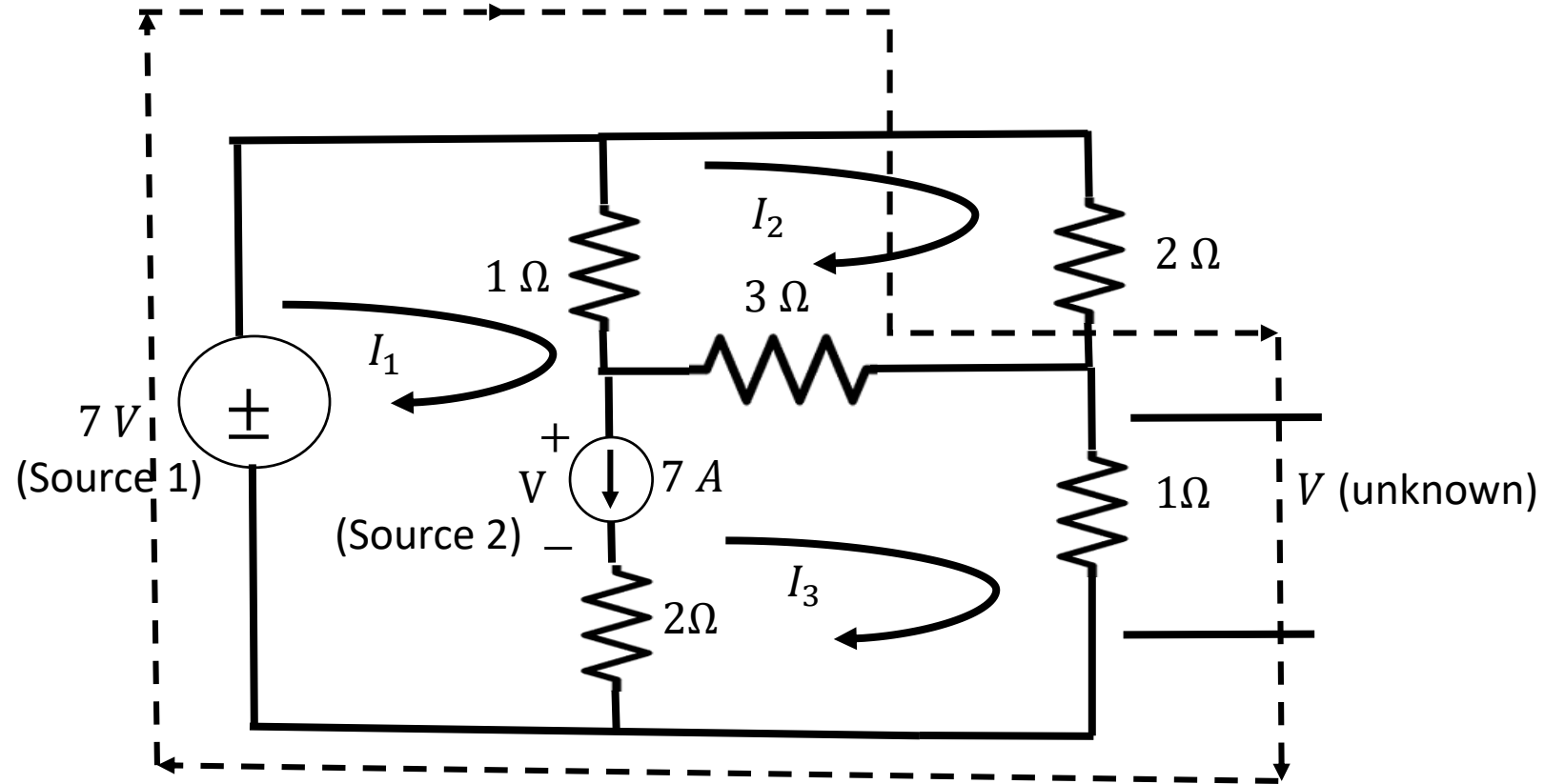

Supermesh Analysis Example

Since voltage across 7 A source is not clear so we need to avoid this branch.

So we take the 'union' of node 1 & 3 and then proceed.

Now, moving clockwise for left bottom corner, we get

$$-7 + (I_1 - I_2) \cdot 1 + (I_3 - I_2) \cdot 3 + I_3 \cdot 1 = 0 \quad (1) \quad (\text{all voltage drops adding to zero})$$

In mesh 2, we get

$$(I_2 - I_1) \cdot 1 + 2 \cdot I_2 + (I_2 - I_3) \cdot 3 = 0 \quad (2)$$

and finally to get one more equation, we use the source which forced us to take the detour.

$$\text{We have} \quad I_1 - I_3 = 7 \quad (3)$$

Alternately, we can define an extra variable (voltage across the current source)

$$\text{Mesh 1: } -7 + (I_1 - I_2) \cdot 1 + V + 7 \times 2 = 0 \quad (1')$$

$$\text{Mesh 2: } (2) \quad \leftarrow \text{-----} \rightarrow \quad (2')$$

$$\text{Mesh 3: } (I_3 - I_2) \cdot 3 + I_3 \cdot 1 - 2 \times 7 - V = 0 \quad (3')$$

$$\text{4th equation: } I_1 - I_3 = 7$$


Solution:

$$I_1 = 9 \text{ A}$$

$$I_2 = 2.5 \text{ A}$$

$$I_3 = 2 \text{ A}$$


Superposition Theorem

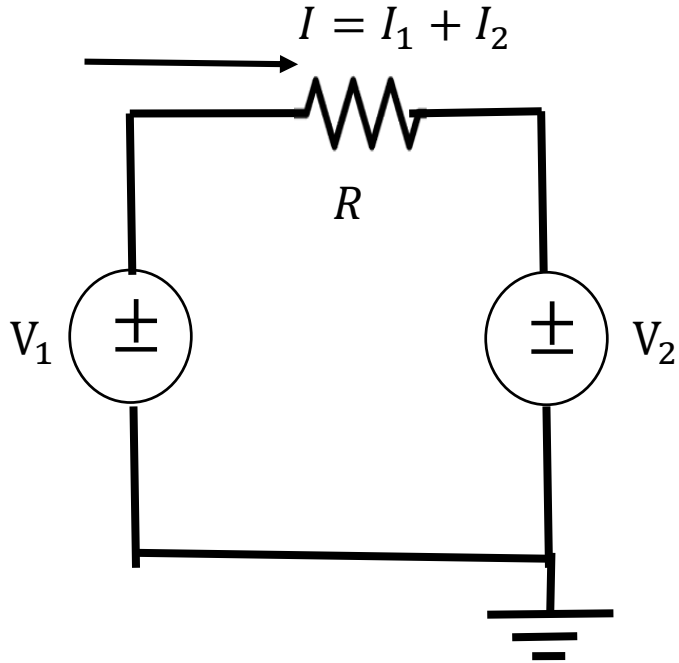

$$I = \frac{V_1 - V_2}{R}$$

$$I_1 (\text{current due to } V_1 \text{ alone}) = \frac{V_1}{R}$$
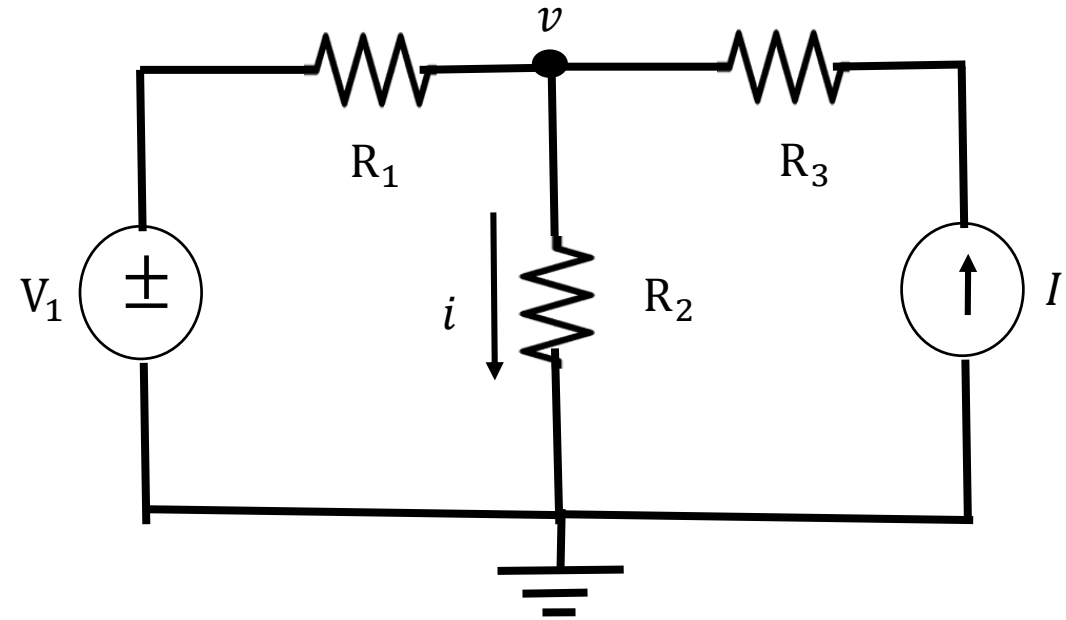
$$I_2 (\text{current due to } V_2 \text{ alone}) = -\frac{V_2}{R}$$



To compute v and i

Superposition Theorem

$$\frac{V-v}{R_1} + I = \frac{v}{R_2} \text{ or } \frac{V}{R_1} + I = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$
$$v = \left(\frac{V}{R_1} + I \right) (R_1 || R_2) = V \cdot \frac{R_2}{R_1 + R_2} + I \cdot \frac{R_1 R_2}{R_1 + R_2}$$

Now let v_1 = contribution of V alone = $V \cdot \frac{R_2}{R_1 + R_2}$ (with current source opened)

v_2 = contribution of I alone = $I(R_1 || R_2)$ (V replaced by a short, i.e. 0 volts)


$$\text{So } v = v_1 + v_2$$

This property holds for all linear circuits.

For linear circuits, superposition principle states that the net current through a given branch or the voltage across a given branch is the algebraic sum of the contribution made by each individual source that acts independently.

Superposition Theorem

Examples of linear systems

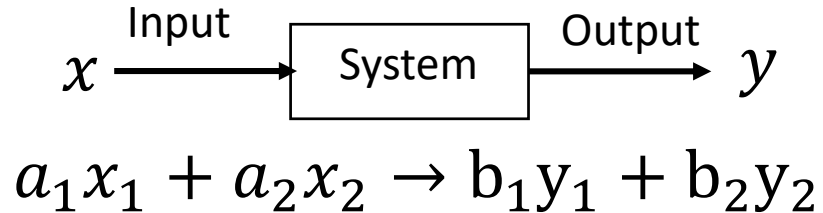

The inputs and outputs could be scalar or vectors.
And vectors they could be finite dimensional or infinite dimensional.

Example 1

Consider all Riemann-integrable functions on the interval $[a, b]$, $f: [a, b] \rightarrow \mathbb{R}$ (real line)

Then, $f_1 \rightarrow \int_a^b f_1(x)dx$ and $f_2 \rightarrow \int_a^b f_2(x)dx$

$$a_1f_1 + a_2f_2 \rightarrow \int_a^b (a_1f_1 + a_2f_2)dx = a_1 \int_a^b f_1dx + a_2 \int_a^b f_2dx$$

Example 2

$$\begin{bmatrix} x_1 \\ \vdots \\ x_n \end{bmatrix} \in \mathbb{R}^n, A: \mathbb{R}^n \rightarrow \mathbb{R}^m$$

$Ax = y$ is a linear transformation


As

$$\begin{aligned} A(a_1x_1 + a_2x_2) &= a_1Ax_1 + a_2Ax_2 \\ &= a_1y_1 + a_2y_2 \end{aligned}$$

$y(t) \triangleq \int h(t - \tau)x(\tau)d\tau$ is a mapping from $x(t) \rightarrow y(t)$
Where $h(\cdot)$ is the so called impulse response of an LTI system.

Superposition Theorem

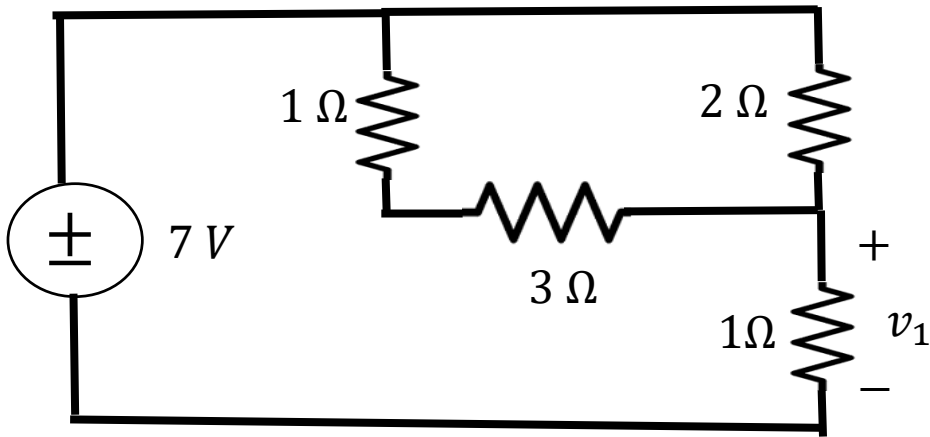
Let us solve the previous example of super mesh analysis through superposition theorem.



Retaining source 1

$$v_1 = 7 \cdot \left[\frac{1}{1 + (4 \parallel 2)} \right] = \frac{7}{1 + 8/6} = \frac{7 \times 6}{14}$$

$v_1 = 3 \text{ volts}$

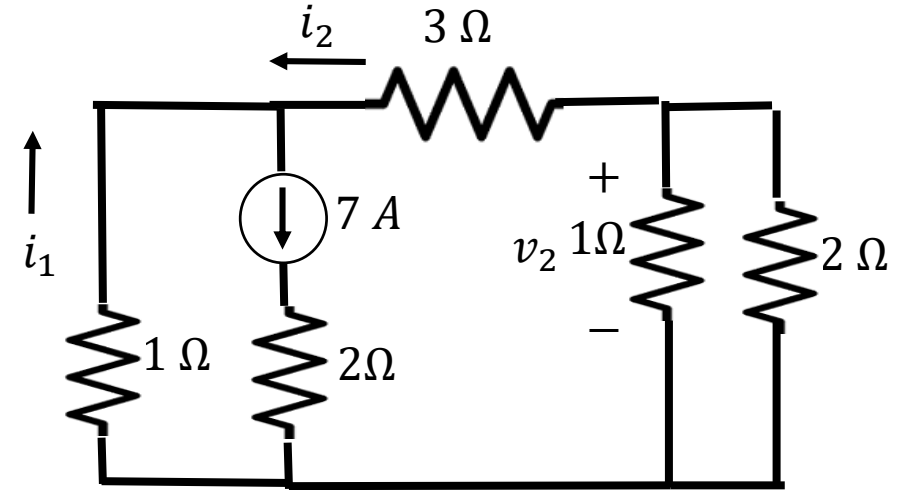

Retaining source 2

$$i_1 + i_2 = 7 \text{ A}$$

$$v_2 = -(2 \parallel 1)i_2 = -\frac{2}{3}i_2$$

$$i_2 = \frac{7 \cdot (1)}{1 + 3 + (1 \parallel 2)} = \frac{7}{4 + 2/3} = \frac{3}{2} \text{ A}$$


$$v_2 = -\frac{2}{3} \times \frac{3}{2} = -1 \text{ V}$$

$$v = v_1 + v_2 = 2 \text{ V}$$


Verify that $i_3 = 2 \text{ A}$

Thevenin equivalent circuit

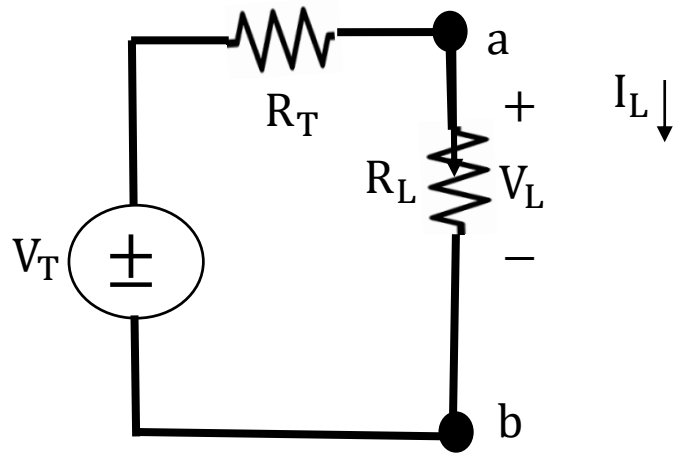For linear circuits where principle of superposition applies, Thevenin equivalent of a circuit between a pair of terminals is a two parameter characterization .


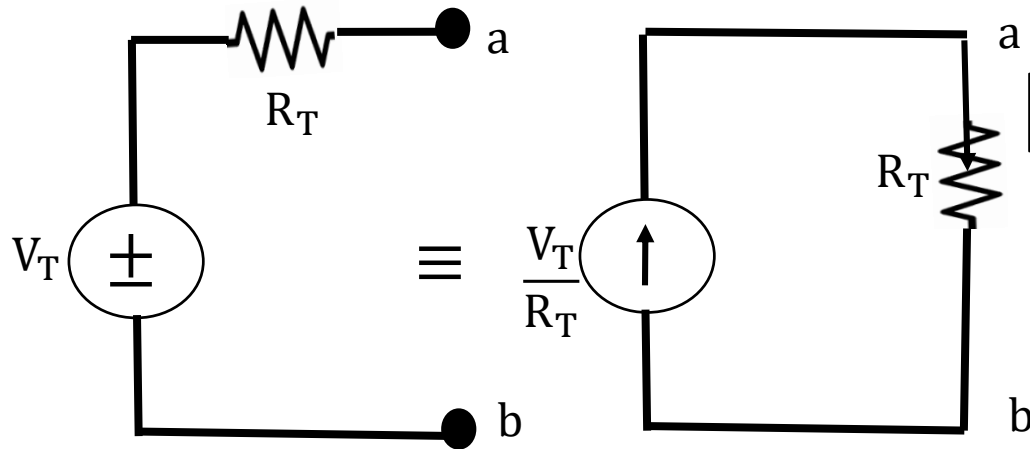
$$V_L = I_L R_L$$
$$R_L \rightarrow +\infty \Rightarrow V_{ab} = V_{oc} = V_T \text{ (max voltage, min current)}$$
$$R_L = 0 \Rightarrow I_{ab} = I_{sc} = I_T = \frac{V_T}{R_T} \text{ (max current, min voltage)}$$
$$R_T = \frac{V_{oc}}{I_{sc}}$$




Norton's Equivalent

Sometimes looking backwards, after suppressing all independent sources, one can easily compute R_T , generally with the help of series/parallel connections

Thevenin equivalent circuit

- Through superposition, we simplify the problem or decompose it into a set of simpler problems.
- While computing Thevenin equivalent we are using linearity to reduce the problem into two subproblems.
- These sub problems are defined by two extreme or limiting cases,
 - Computing the open circuit voltage ($R_L \rightarrow +\infty$)
 - Computing the short circuit current ($R_L = 0$)
- By doing so, we can focus our attention on the load itself.
- Readings
 - *Dimitri P. Betsekas* (1996), “Thevenin decomposition & large-scale optimization”, *J.O.T.A.*, Vol. 89, pp 1-15.
 - *Gorazza, G.C., Saveda C.G., & Lengo G.*, “Generalized Thevenin’s theorem for linear n-port networks”, *IEEE transactions on circuit theory*, Vol. 16, pp 564-566, 1969.

Thevenin equivalent circuit examples

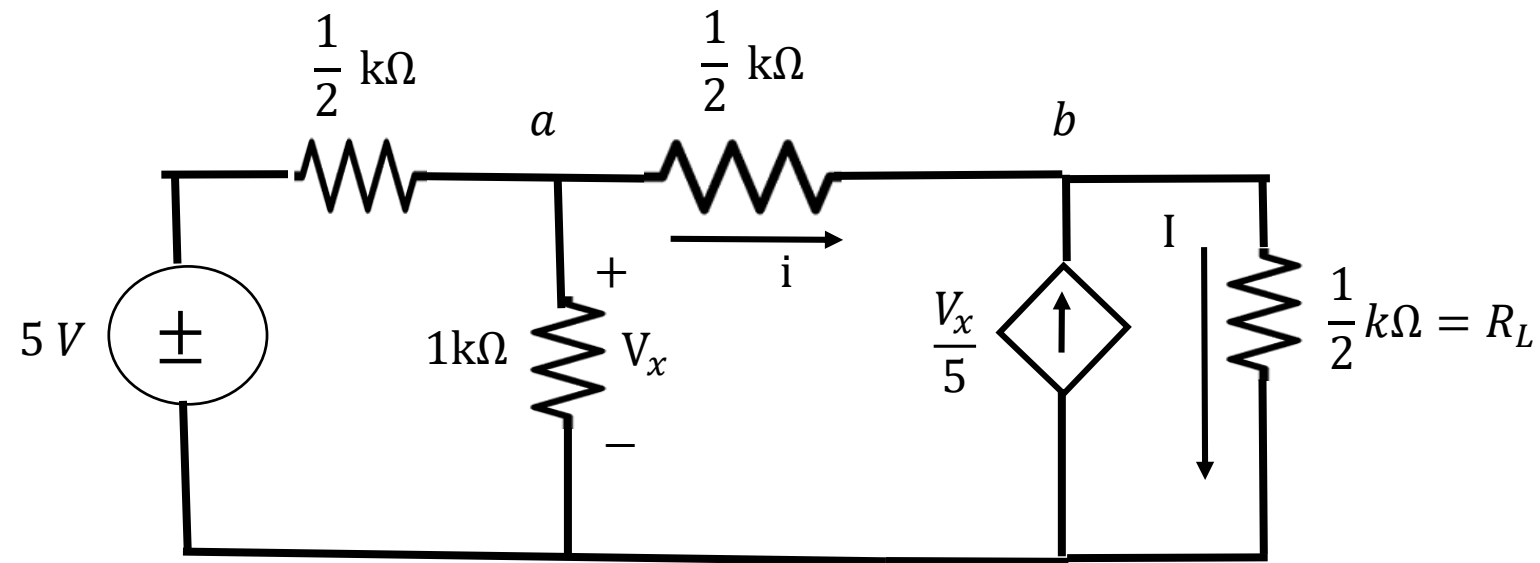

To compute I , we have to compute V_T , R_T with respect to R_L

Thevenin equivalent circuit examples

For V_{oc} , we open the resistance across R_L and then apply KCL at point 'a'

We have, $\frac{5-V_x}{1/2} = \frac{V_x}{1} - \frac{V_x}{5} = \frac{4}{5}V_x$

On solving, we get $5 - V_x = \frac{2}{5}V_x \Rightarrow V_x = \frac{5 \times 5}{7} = \frac{25}{7}$

$$\Rightarrow V_b = V_x + \frac{V_x}{5} \times \frac{1}{2} = \frac{11}{10}V_x = \frac{11 \times 25}{10 \times 7} = \frac{55}{14} = V_{oc}$$

For I_{sc} , we short the resistance across R_L

We can observe that, $I_{sc} = \frac{V_x}{5} + i$


On solving, we get $V_x = \frac{5 \times (1 || \frac{1}{2})}{\frac{1}{2} + (1 || \frac{1}{2})} = \frac{5 \times \frac{1}{2}}{\frac{3}{2} \times (\frac{1}{2} + \frac{1}{3})} = \frac{5}{5/2} = 2 \text{ V}$

$$I_{sc} = \frac{2}{5} + \frac{2}{1/2} = \frac{22}{5}$$

The Thevenin resistance is given by, $R_T = \frac{V_{oc}}{I_{sc}} = \frac{55 \times 5}{14 \times 22} = \frac{25}{28} \text{ k}\Omega$


The current through R_L , $I = \frac{V_{oc}}{R_T + 1/2} = \frac{55/14}{\frac{25}{28} + \frac{1}{2}} = \frac{55 \times 2}{25 + 14} = \frac{110}{39} \text{ mA}$

Thevenin equivalent circuit examples

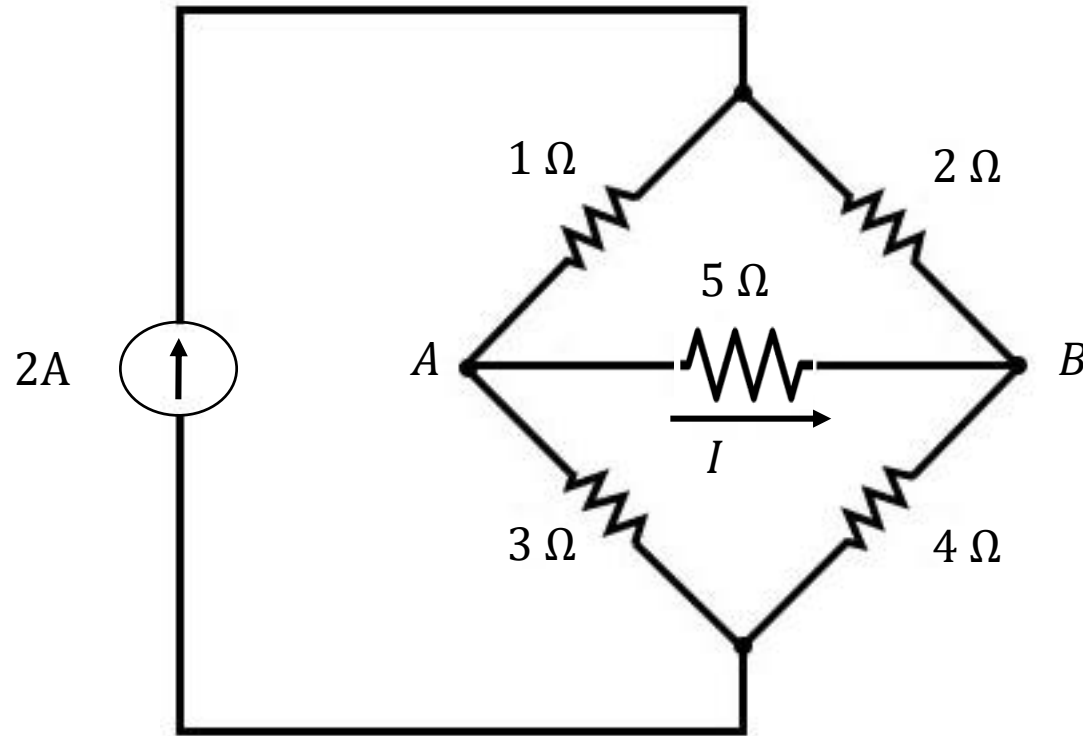

Compute I using Thevenin equivalent circuit

Thevenin equivalent circuit examples

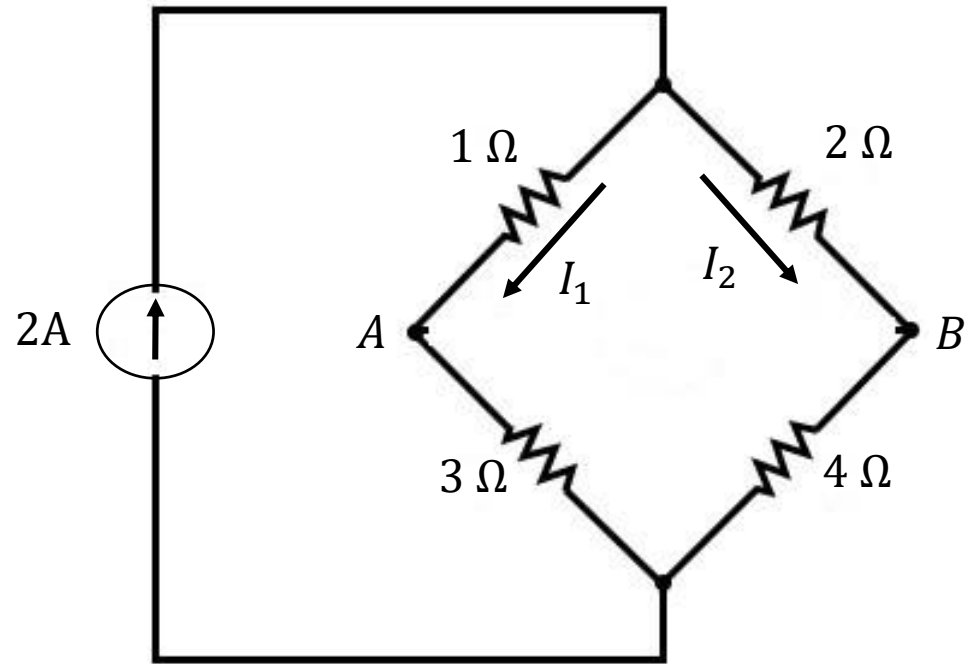

For calculating open circuit voltage V_{oc} or V_T

We have to find $V_{AB} = V_A - V_B$


$$I_1 = \frac{2 + 4}{2 + 4 + 1 + 3} \times 2 = \frac{6}{5} A$$

$$I_2 = 2 - I_1 = \frac{4}{5} A$$

$$V_{AB} = V_A - V_B = 3I_1 - 4I_2$$

$$V_{AB} = 3.6 - 3.2 = 0.4 V$$

Thevenin equivalent circuit examples

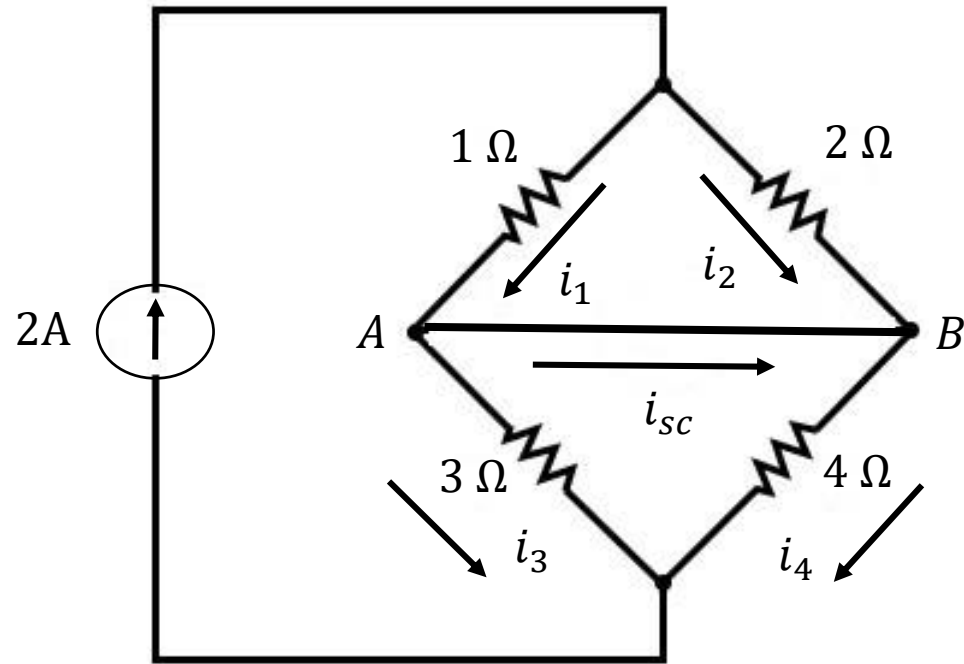

For calculating short circuit current I_{sc} or V_T

$$i_1 = \frac{2 \times 2}{2+1} = \frac{4}{3} \text{ A}, i_3 = \frac{4 \times 2}{3+4} = \frac{8}{7} \text{ A}$$


$$\Rightarrow I_{sc} = \frac{4}{3} - \frac{8}{7} = \frac{4}{21} \text{ A}$$

$$\therefore \text{Thevenin resistance, } R_T = \frac{V_{oc}}{I_{sc}} = \frac{2}{5} \times \frac{21}{4} = \frac{42}{20} = 2.1$$

$$\text{We can also verify } R_T = (3 + 4) \parallel (1 + 2) = \frac{7 \times 3}{10} = 2.1 \Omega$$

Thevenin equivalent circuit

$$V_T = \frac{2}{5} \text{ V}$$

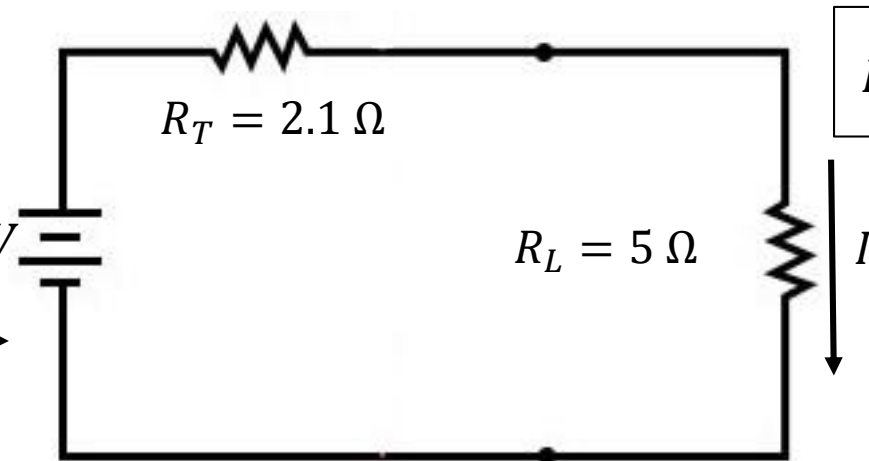

$$I = \frac{0.4}{2.1 + 5} = 56.3 \text{ mA}$$