

1. In the given circuit find the current through the 4 Ohm resistor. Also comment on the unrealistic nature of this circuit.

nature of this circuit.

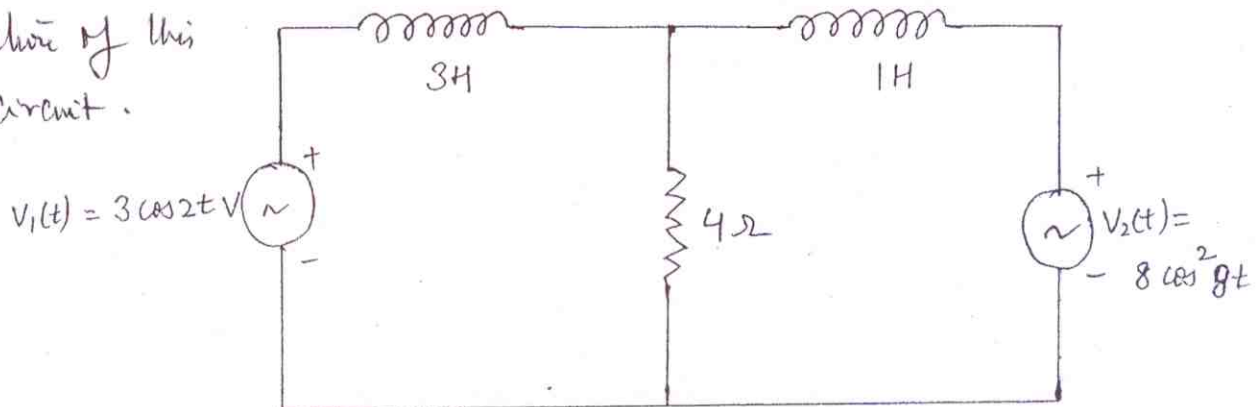


Fig 1

2. Calculate the current  $I_x$  using Thevenin's theorem.

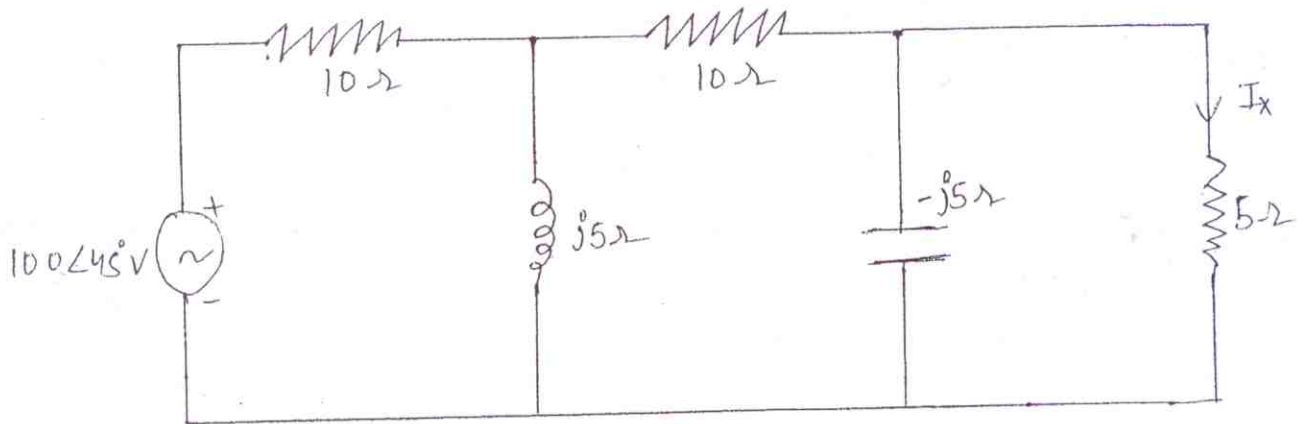


Fig 2

3. Determine the current through the  $j10 \text{ ohm}$  reactance by nodal method, mesh/loop method & Superposition theorem.


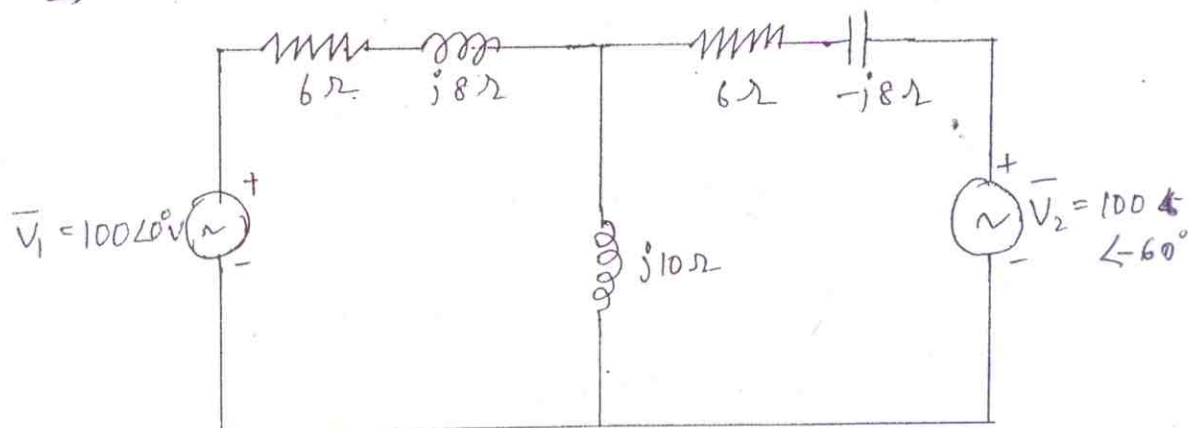


Fig 3

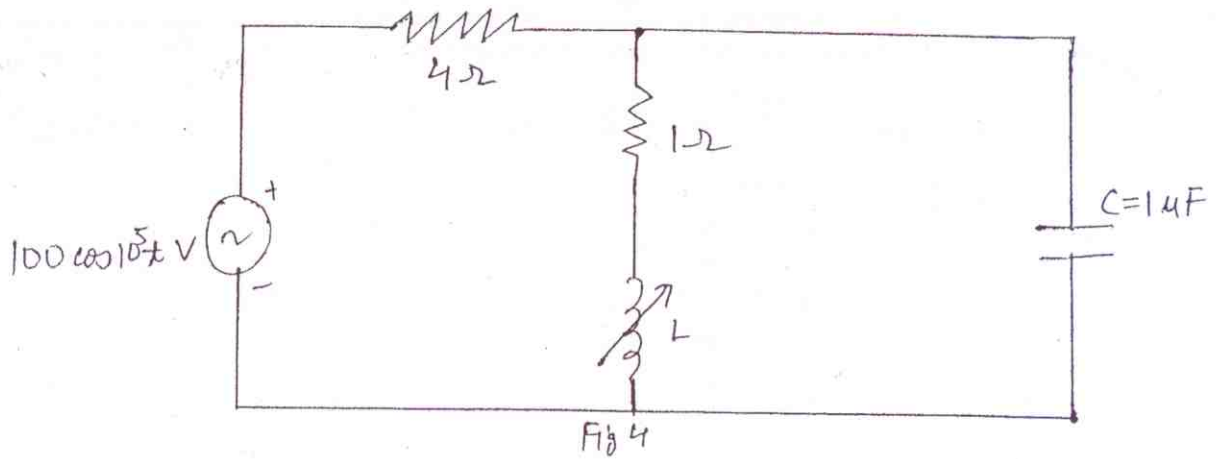4. (a) Find the value of  $L$  for which the steady state voltage across it is maximum.  
 (b) For the value of  $L$  determined in (b), find the magnitude of phasor voltage across  $L$ .



5. In the given circuit, determine the currents  $i_1$  and  $i_2$ .

