


Introduction to Electronics

- Man's interaction with nature and systems designed by him is an interplay of energy and information.
- Contrast between the notion of a *source* in *circuits* v/s *information theory*.
- In 80's consumption of energy/person in USA was 75 times that of India and served as a benchmark of advancement.
- In current times, usage of information plays a dominant role .
- In 1956, white collar workers in USA acceded blue collar workers.
- Information age started around 1990, although information theory as a discipline began in 1948.
- Professor Gallager of MIT while visiting IIT Bombay in 2008, shared with me that theoretical developments in information theory had little impact for first 3 decades whereas in subsequent years the theoretical results have had a major impact on practice.
- Take compression and error correcting codes as examples.

Introduction to Electronics

- In this course, our focus will be on basic **circuit analysis**
- In particular, it will deal with basic concepts related to circuits made up of components / elements such as resistors, inductors, capacitors, diodes, transistors, operational amplifiers, logic gates and flip-flops as memory devices
- These circuits give rise to systems achieving objectives in terms of control, communication, storage, retrieval of information, computing and so on.
- Telegraph and *Morse code* (a compact representation of text) came into existence long before light *bulb* was invented by Edison
- **Transistor** in **1948** was developed at AT &T labs in response to the need of communication industry for an effective **switch**.
- 1948 also marks the birth of ***information theory*** which guides our advancement into information age.

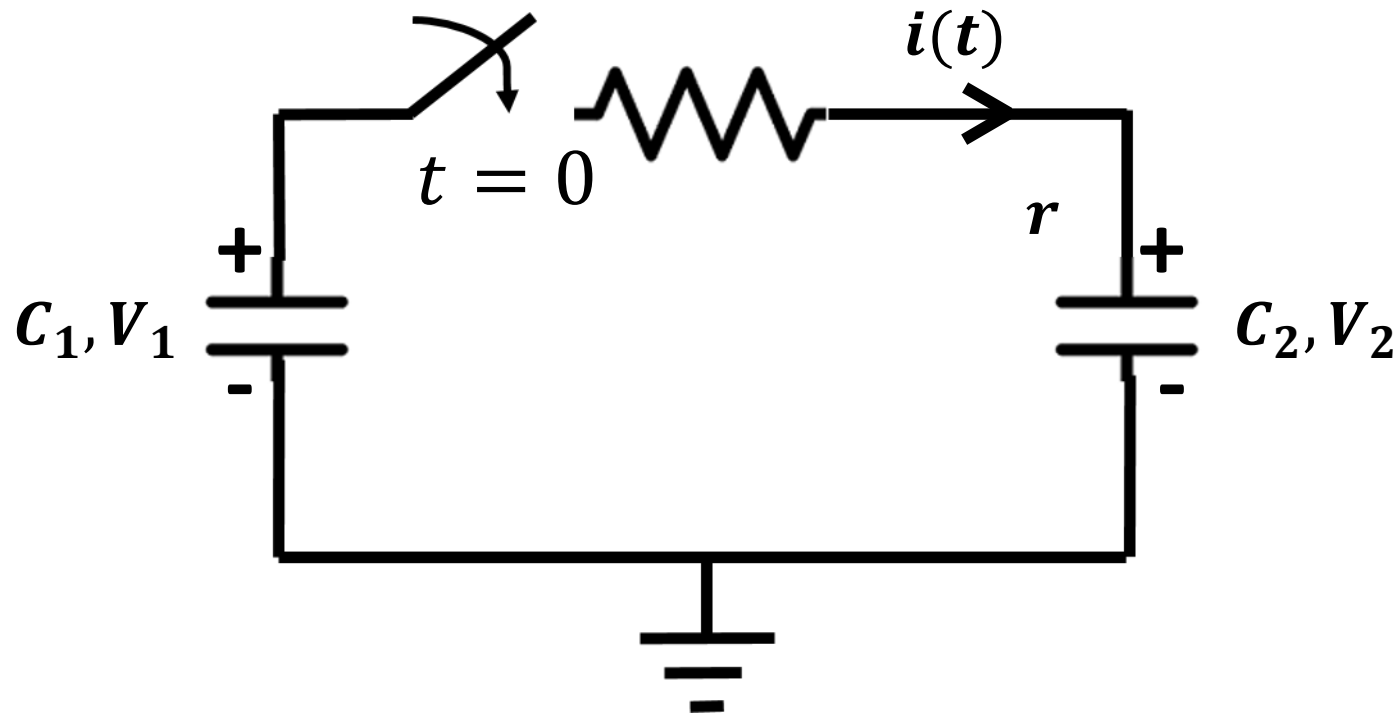Conservation of energy v/s Conservation of charge



Let $V_1 > V_2$

$$i(t) = \frac{v_1(t) - v_2(t)}{r}$$

$$i(\infty) = 0 \text{ and } v_1(\infty) = v_2(\infty) = V \text{ (say)}$$

Conservation of energy v/s Conservation of charge

By conservation of charge,
 $C_1 V_1 + C_2 V_2 = (C_1 + C_2)V$



$$V = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2$$

(a convex combination of V_1 and V_2)

$$\text{Initial energy} = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = E_1, \quad \text{Final energy} = \frac{1}{2} (C_1 + C_2) V^2 = E_2$$

$$\text{Final energy} = \frac{1}{2} (C_1 + C_2) \left[\left(\frac{C_1}{C_1 + C_2} \right)^2 V_1^2 + \left(\frac{C_2}{C_1 + C_2} \right)^2 V_2^2 + \frac{2C_1 C_2}{C_1 + C_2} V_1 V_2 \right]$$
$$\longrightarrow E_1 = \frac{1}{2} (C_1 + C_2) \left[\left(\frac{C_1}{C_1 + C_2} \right) V_1^2 + \left(\frac{C_2}{C_1 + C_2} \right) V_2^2 \right] > E_2$$

$$\text{As } V^2 < \frac{C_1}{C_1 + C_2} V_1^2 + \frac{C_2}{C_1 + C_2} V_2^2 \quad \text{by Jensen's inequality}$$

Jensen's Inequality

$$\phi\left(\sum_{i=1}^{i=n} a_i x_i\right) \leq \sum_{i=1}^{i=n} a_i \phi(x_i)$$

where $0 \leq a_i \leq 1$, $\sum_{i=1}^{i=n} a_i = 1$,
and $\phi(\cdot)$ is a concave upward function.
eg. $\phi(x) = x^2$.

Conservation of energy v/s Conservation of charge

Optional problem: difference is **dissipated** energy through r

Verify that $\int_0^\infty i(t)^2 r dt = E_1 - E_2$ is independent of r .

Note that $i(t) = C_2 \frac{dv_2(t)}{dt} = -C_1 \frac{dv_1(t)}{dt} = \frac{v_1(t) - v_2(t)}{r}$

$$-\frac{dv_2(t)}{dt} = -\frac{i(t)}{C_2}, \quad \frac{dv(t)}{dt} = -\frac{i(t)}{C_1}$$

$$\frac{d(v_1(t) - v_2(t))}{dt} = -i \left[\frac{1}{C_1} + \frac{1}{C_2} \right] = \frac{-(v_1(t) - v_2(t))}{r(C_1 || C_2)}$$

Let $v_1(t) - v_2(t) = v(t)$

Then $\frac{dv(t)}{dt} = -\frac{v(t)}{rC}$ where $C = \frac{C_1 C_2}{C_1 + C_2}$

$$\text{Or } \int_{V_1 - V_2}^{v(t)} \frac{dv(t)}{v(t)} = -\frac{1}{rC} \int_0^t dt$$

$$\text{Or } -\frac{t}{rC} = \log v(t) - \log(V_1 - V_2)$$

$$= \log \left(\frac{v(t)}{V_1 - V_2} \right)$$

$$\text{Or } v(t) = (V_1 - V_2) \exp^{-\frac{t}{rC}} \rightarrow 0 \text{ as } t \rightarrow \infty.$$

Conservation of energy v/s Conservation of charge

Optional problem: difference is dissipated energy through r

$$\begin{aligned}\int_0^\infty p(t) dt &= \int_0^\infty \frac{v(t)^2}{r} = \frac{(V_1 - V_2)^2}{r} \int_0^\infty \exp^{-\frac{2t}{rC}} dt \\ &= -\frac{(V_1 - V_2)^2}{r} \frac{rC}{2} e^{-\frac{2t}{rC}} \Big|_0^\infty \\ &= \frac{1}{2} C (V_1 - V_2)^2 = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2\end{aligned}$$

Since $E_1 - E_2$ is independent of r ,

we have $\lim_{\{r \rightarrow 0\}} (E_1 - E_2) = E_1 - E_2$

If $r = 0$ before switch closes, the energy will radiate.

If $V_2 < 0$, then both capacitors have potential in same direction.

$$\text{Then } i(t) = C_2 \frac{dv_2(t)}{dt} = C_1 \frac{dv_1(t)}{dt} = \frac{v_1(t) + v_2(t)}{r}$$

$$\text{Or } \frac{i(t)}{C_1} + \frac{i(t)}{C_2} = \frac{d(v_1(t) + v_2(t))}{dt} =$$

$$\frac{(v_1(t) + v_2(t))(C_1 + C_2)}{r C_1 C_2}$$

$$\text{And } v(t) = v_1(t) + v_2(t) = (V_1 + V_2) e^{-\frac{t}{\tau}}$$

$$\text{Where } \tau = \frac{C_1 C_2}{C_1 + C_2} r.$$

Conservation of energy v/s Conservation of charge

Optional problem: difference is dissipated energy through r

$$\text{Again } \int_0^\infty p(t) dt = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 + V_2)^2$$

Since $v_1(t) + v_2(t) \rightarrow 0$ as $t \rightarrow \infty$.

Let V_1' & V_2' be the final voltages on C_1 & C_2 .

$$\text{Then } V_1' + V_2' = 0 \longrightarrow V_1' = -V_2'$$

$$\text{Or } V_1'^2 = V_2'^2$$

$$\text{Final energy} = \frac{1}{2} C_1 V_1'^2 + \frac{1}{2} C_2 V_2'^2 = \frac{1}{2} (C_1 + C_2) V'^2$$

$$\text{Where } |V_1'| = |V_2'| = |V'|$$

By direct computation,

$$\begin{aligned} V_1' &= V_1 - \frac{Q_1}{C_1} = V_1 - \frac{1}{C_1} \int_0^\infty i(t) dt \\ &= V_1 - \frac{(V_1 + V_2)}{rC_1} \int_0^\infty e^{-\frac{t}{\tau}} dt = V_1 - \frac{(V_1 + V_2)}{C_1} C_{eq} \\ &= V_1 - \frac{(V_1 + V_2)C_2}{C_1 + C_2} = \frac{V_1 C_1}{C_1 + C_2} - \frac{V_2 C_2}{C_1 + C_2} \end{aligned}$$

Conservation of energy v/s Conservation of charge

Optional problem: difference of initial and final energy is dissipated energy through r.


$$\text{Then } V_2' = V_2 - \frac{(V_1 + V_2)C_{eq}}{C_2} = \frac{V_2 C_2}{C_1 + C_2} - \frac{V_1 C_1}{C_1 + C_2} = -V_1'$$

If $C_1 V_1 = C_2 V_2$ then $V_1' = V_2' = 0$ and net charge on

individual capacitors is zero or the two capacitors discharge completely.

Conservation of energy, *the dual problem*

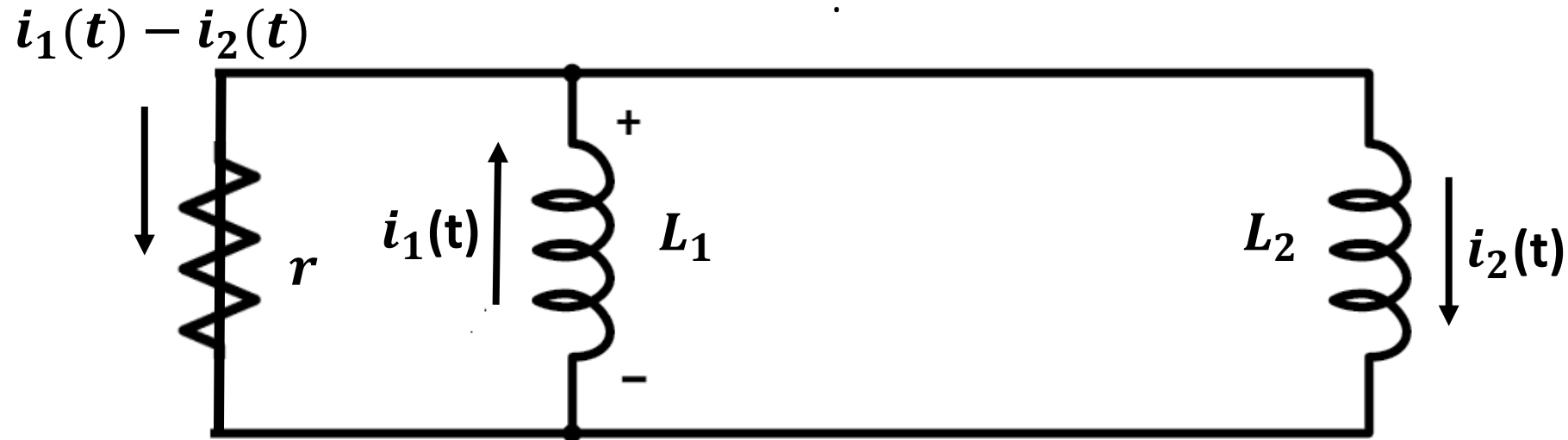Let following configuration come into place at $t=0$, with initial currents I_1 and I_2 .



$$p(t) = (i_1(t) - i_2(t))^2 r$$

$$\begin{aligned} -L_1 \frac{di_1(t)}{dt} &= L_2 \frac{di_2(t)}{dt} = (i_1(t) - i_2(t))r \\ -\frac{di_1(t)}{dt} &= (i_1(t) - i_2(t)) \frac{r}{L_1}, \\ \frac{di_2(t)}{dt} &= (i_1(t) - i_2(t)) \frac{r}{L_2} \end{aligned}$$

Conservation of energy

The Dual problem

$$\frac{d(i(t) - i_2(t))}{dt} = -r \left[\frac{1}{L_1} + \frac{1}{L_2} \right] (i_1(t) - i_2(t))$$

$$\text{Or } \frac{di(t)}{dt} = -\frac{r}{L_1 || L_2} i(t) = -\frac{i(t)}{\tau} \quad \text{where } \tau = \frac{(L_1 || L_2)}{r}$$

$$\Rightarrow \int \frac{di(t)}{i(t)} = - \int \frac{dt}{\tau}$$

$$\text{Or } \ln i(t) - \ln i(0) = -\frac{t}{\tau} = \ln \left(\frac{i(t)}{i(0)} \right)$$

$$i(t) = I e^{-\frac{t}{\tau}} \rightarrow 0 \text{ as } t \rightarrow \infty,$$

where $I = I_1 - I_2$.

Conservation of energy

The Dual problem

$$\begin{aligned}\int p(t)dt &= \int i(0)^2 r e^{-\frac{2t}{\tau}} dt = \frac{i(0)^2 r e^{-\frac{2t}{\tau}}}{-\frac{2}{\tau}} \Big|_0^\infty = \frac{\tau \cdot r}{2} i(0)^2 \\ &= \frac{1}{2} (L_1 || L_2) (I_1 - I_2)^2\end{aligned}$$

So in steady state,


$$E = \frac{1}{2} (L_1 + L_2) I^2 = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - \frac{1}{2} (L_1 || L_2) (I_1 - I_2)^2.$$

Exercise : Think about the situation when in steady state ,
zero current flows through each inductor.

Power sources and elements

Charge, Current, Voltage, Power

q $\frac{dq}{dt}$ $v(t)$ $p(t)$

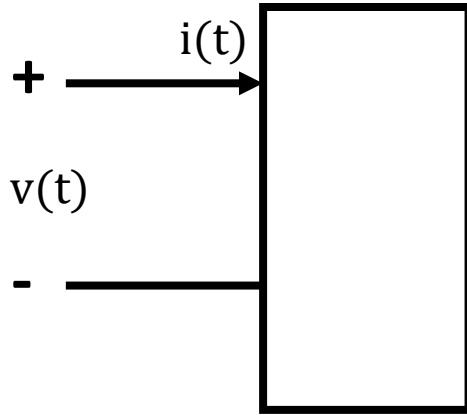





Power absorbed

$p(t) = v(t)i(t) > 0$ if either $v(t), i(t) > 0$ or $v(t), i(t) < 0$

Independent Sources





Voltage

Current

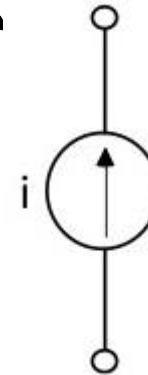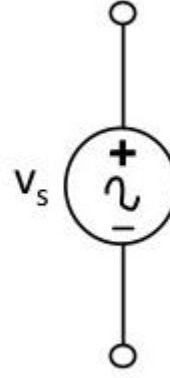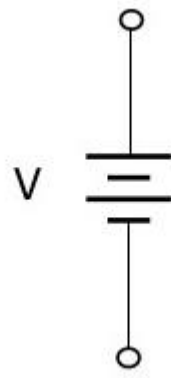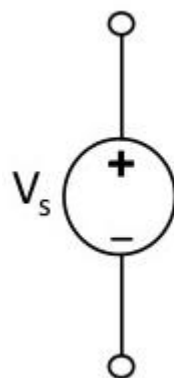

Power sources and elements

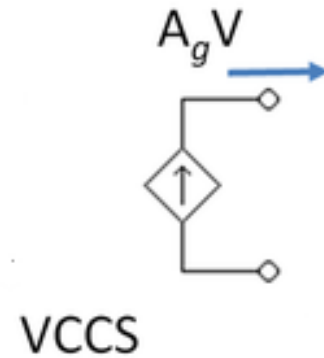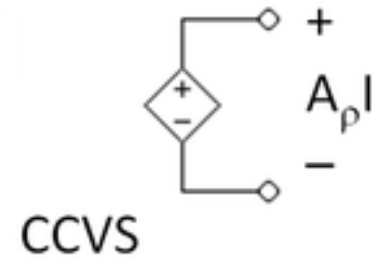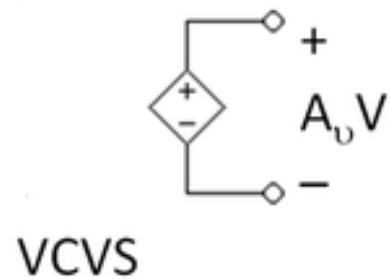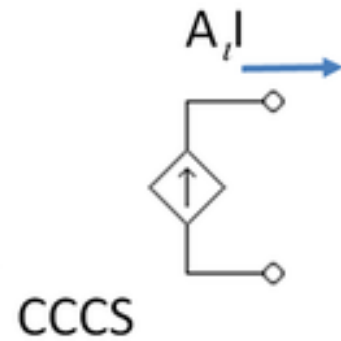
Dependent Sources:
current / voltage controlled current / voltage sources



Kirchhoff's Laws

Kirchhoff's current law (KCL)

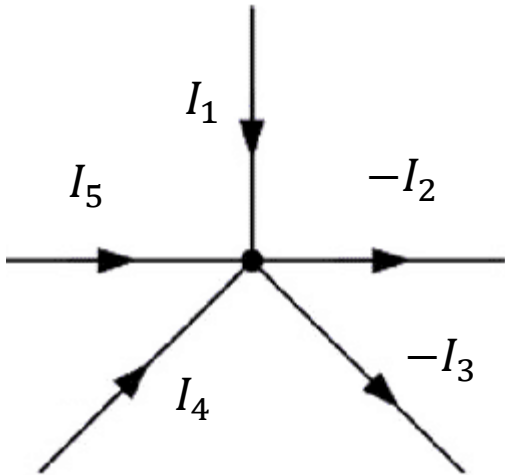- A consequence of *charge* conservation
- Node: a point where two or more elements meet




$$\sum_{j=1}^n I_j = 0$$

(KCL)

Kirchhoff's voltage law (KVL)

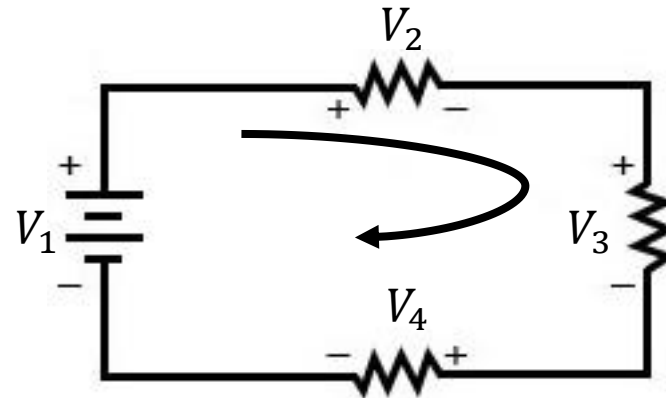
- A consequence of *energy* conservation
- Loop: a closed path starting from a particular node and ending there *without* revisiting that particular node



$$\sum_{i=2}^m V_i = V_1$$

(KVL)

Resistors in series and in parallel

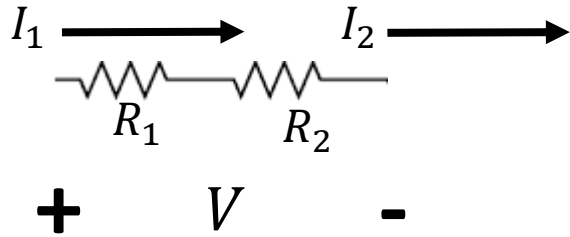


$I_1 = I_2 = I$ (suppose) by KCL

$$V = I_1 R_1 + I_2 R_2 = I(R_1 + R_2)$$

$$\frac{V}{I} = R_1 + R_2$$

The equivalent resistance for n resistors by induction will be given by

$$R_{eq} = \sum_{i=1}^n R_i$$

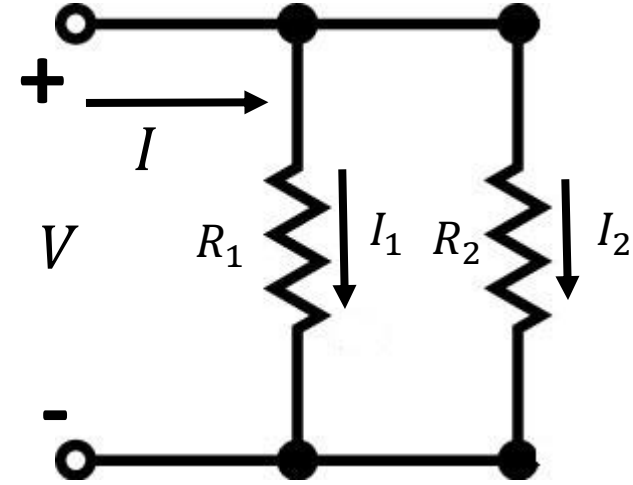

$$V = I_1 R_1 = I_2 R_2$$

$$I_1 + I_2 = I$$

$$V \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = I$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

For n resistors,

$$R_{eq} = \left(\sum_{i=1}^n R_i^{-1} \right)^{-1}$$

A similar approach can be followed for finding equivalent Inductance in series and parallel